

Projeto Multiplicador



Grupo 4: André William Régis, André Neffa, Felipe Borba e Leonardo Gideão

Projeto 1: Multiplicador por Somas Consecutivas

```
begin
file_open(input_buf, "/home/kuru/UFSC/SD/QuartusProjects/TP/multiplier1/inputs.txt", read_mode);
file_open(output_buf, "/home/kuru/UFSC/SD/QuartusProjects/TP/multiplier1/outputs_testbench.txt", write_mode);

wait until reset = '0';

while not endfile(input_buf) loop
    readline(input_buf, read_col_from_input_buf);
    read(read_col_from_input_buf, val_A);
    read(read_col_from_input_buf, val_SPACE);
    read(read_col_from_input_buf, val_B);

    a <= val_A;
    b <= val_B;

    wait for clkp; inicio <= '1';
    wait for clkp; inicio <= '0';

    -- wait for (2**n+3)*clkp; -- Pior caso
    while (pronto = '0') loop -- Roda até sinalizar que possui o resultado
        wait for clkp;
    end loop;

    write(write_col_to_output_buf, saida);
    writeline(output_buf, write_col_to_output_buf);

end loop;

write(write_col_to_output_buf, string("Simulation from testbench completed!"));
writeline(output_buf, write_col_to_output_buf);

file_close(input_buf);
file_close(output_buf);
```

VHDs: Persistência de dados, para realização do testbench.

multiplier_tb.vhd

Projeto 1: Multiplicador por Somas Consecutivas

BEGIN

```
mux1: mux2paral
  GENERIC MAP (n => n)
  PORT MAP (saisomasub, entA, ini, saimux1);
regP: registrador_r
  GENERIC MAP (n => n)
  PORT MAP (clk, ini, CP, saisomasub, sairegP);
regA: registrador
  GENERIC MAP (n => n)
  PORT MAP (clk, CA, saimux1, sairegA);
regB: registrador
  GENERIC MAP (n => n)
  PORT MAP (clk, ini, entB, sairegB);
mux2: mux2paral
  GENERIC MAP (n => n)
  PORT MAP (sairegP, sairegA, dec, saimux2);
mux3: mux2paral
  GENERIC MAP (n => n)
  PORT MAP (entB, (0 => '1', others => '0'), dec, saimux3);
somasub: somadorsubtrator
  GENERIC MAP (n => n)
  PORT MAP (saimux2, saimux3, dec, saisomasub);
geraAz: igualazero
  GENERIC MAP (n => n)
  PORT MAP (sairegA, Az);
geraBz: igualazero
  GENERIC MAP (n => n)
  PORT MAP (sairegB, Bz);


saida <= sairegP;
conteudoA <= sairegA;
conteudoB <= sairegB;
```

END estrutura;

VHDs: BO(Bloco Operativo).


bo.vhd

Projeto 1: Multiplicador por Somas Consecutivas

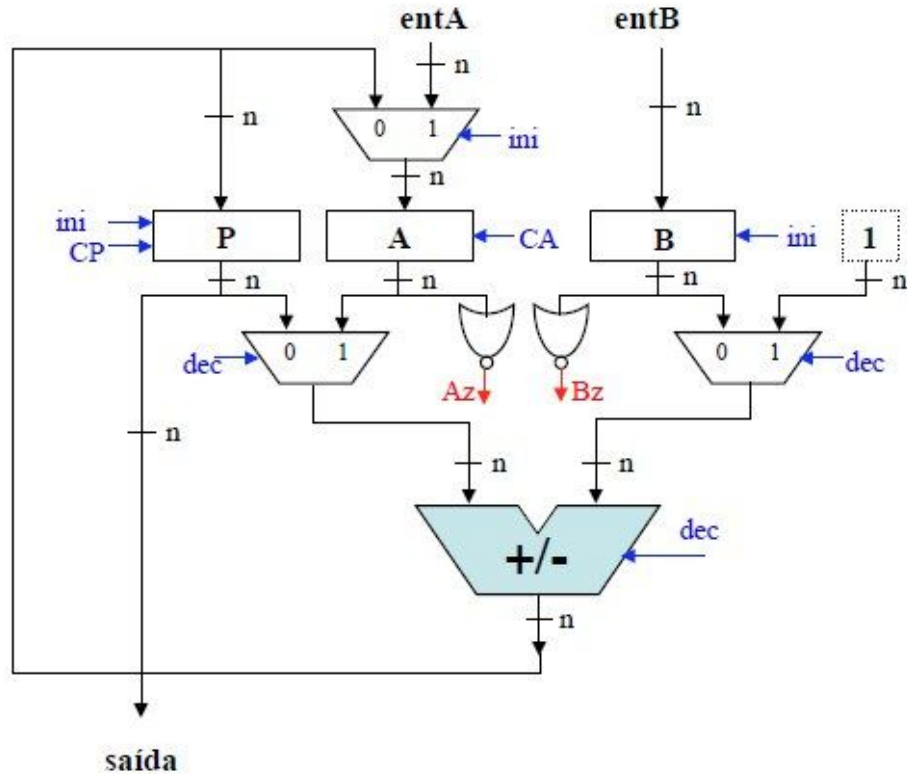


Projeto 1: Multiplicador por Somas Consecutivas

4 bits

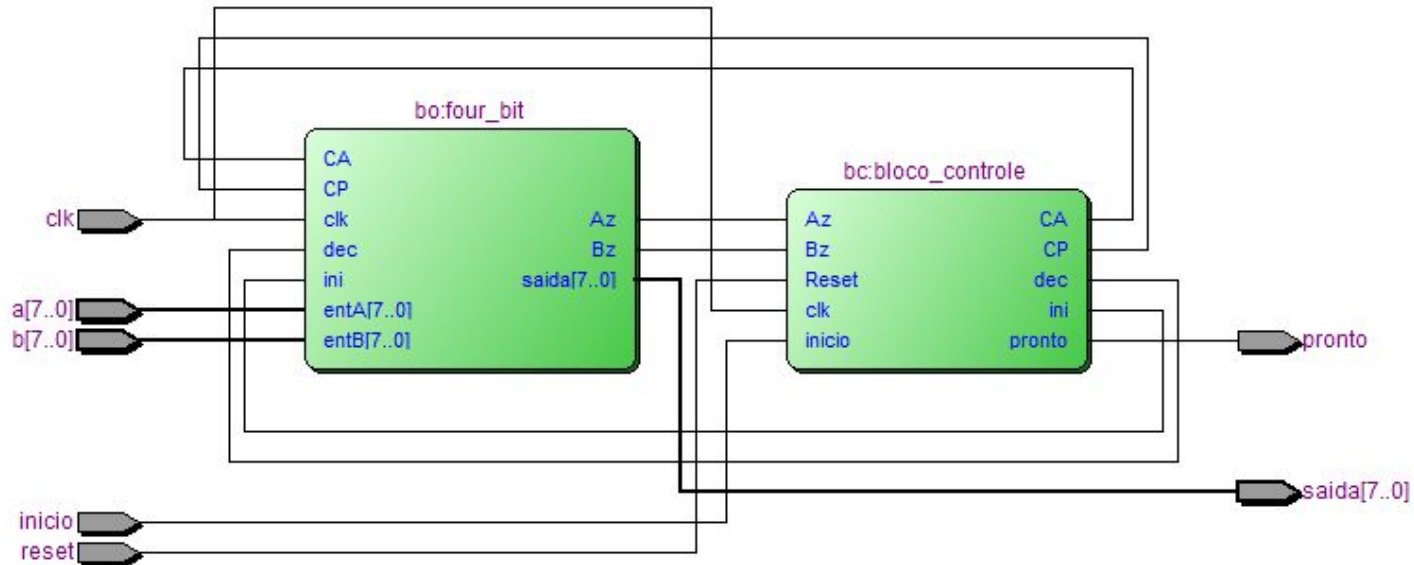


Projeto 1: Multiplicador por Somas Consecutivas

4 bits

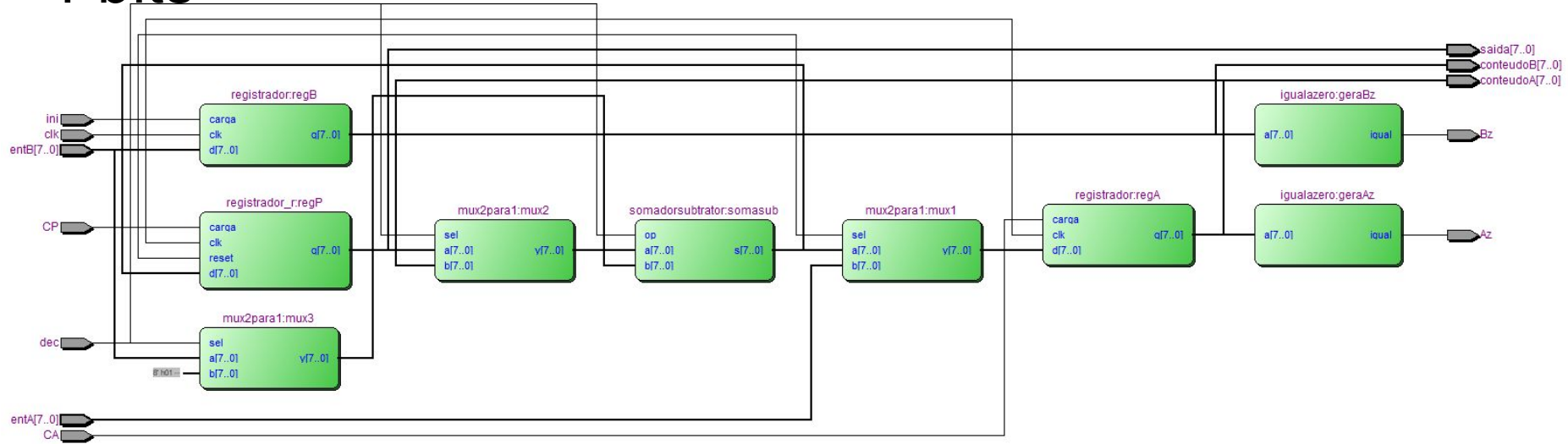


Projeto 1: Multiplicador por Somas Consecutivas

4 bits

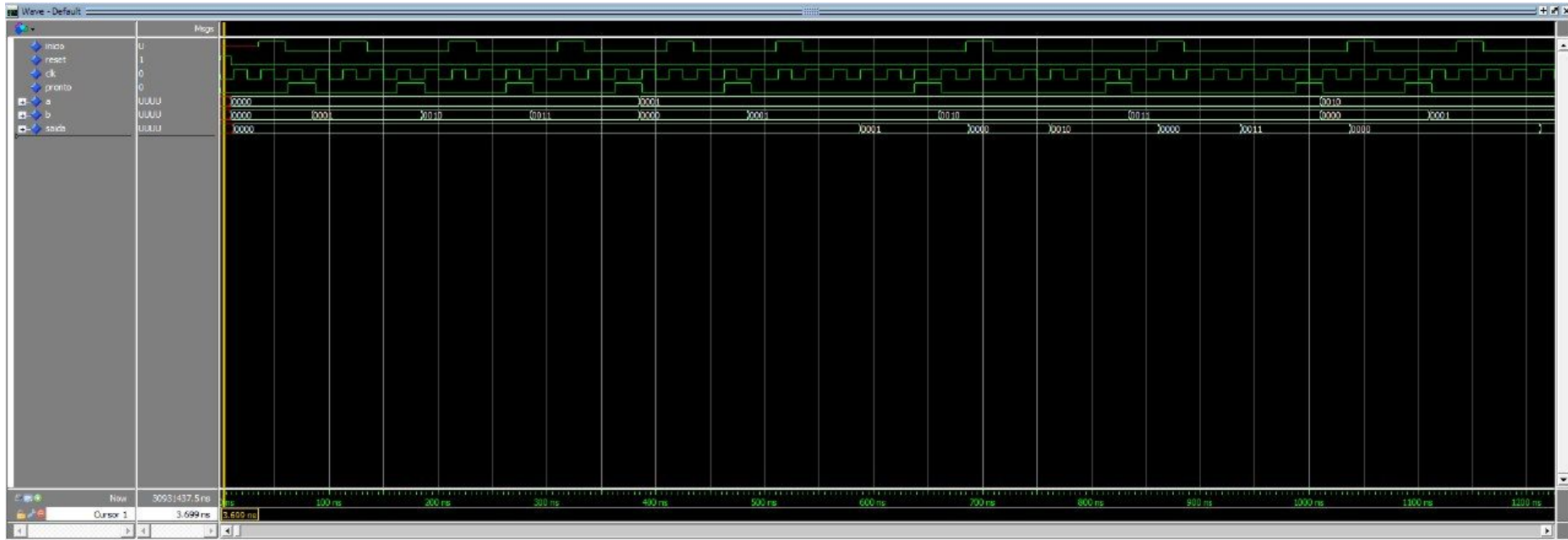


Projeto 1: Multiplicador por Somas Consecutivas

8 bits

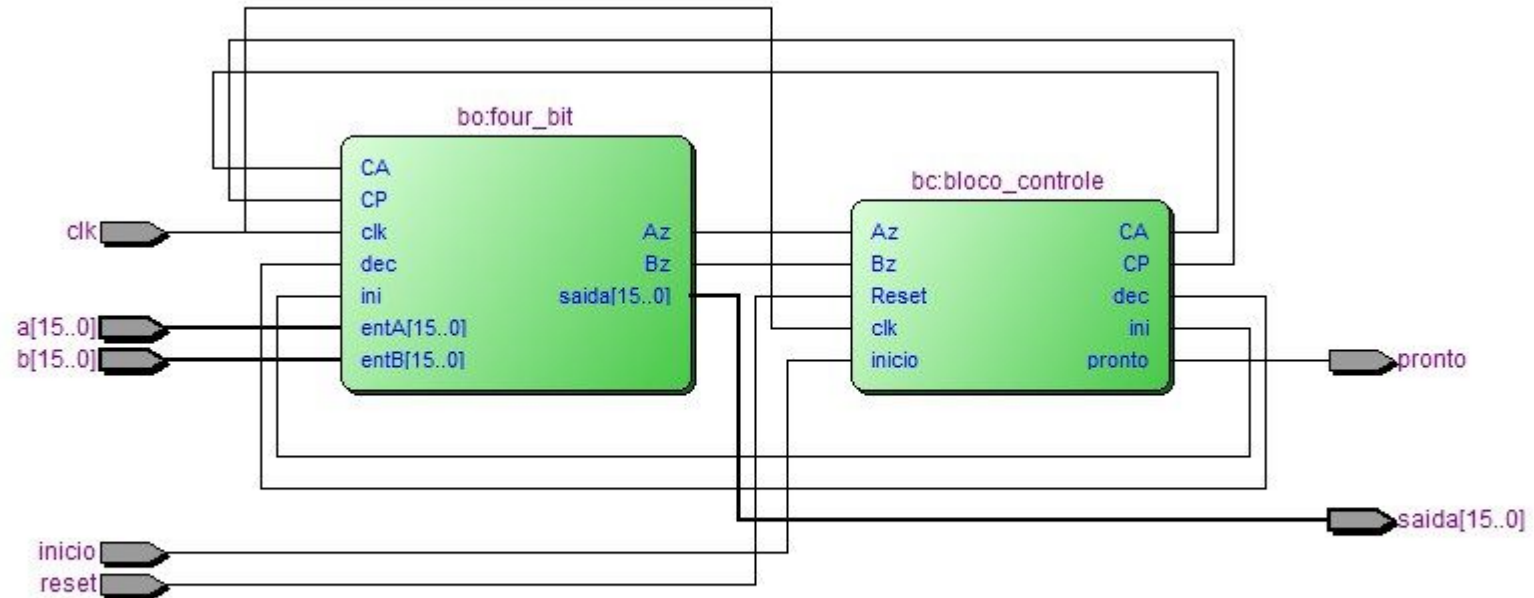


Projeto 1: Multiplicador por Somas Consecutivas

8 bits

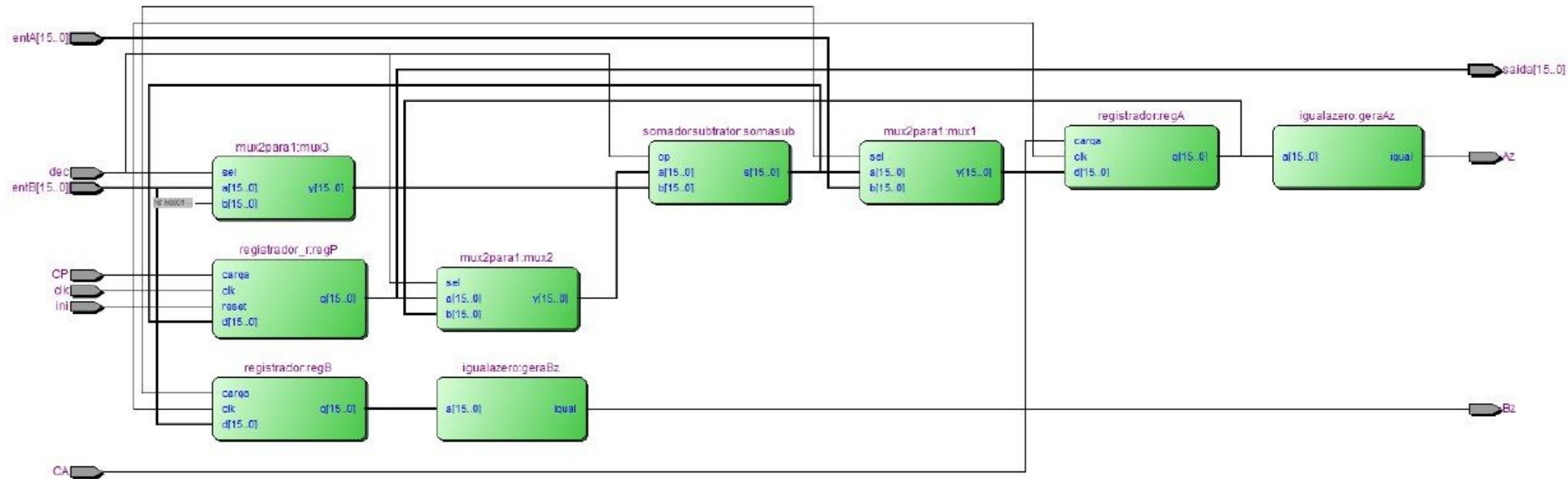

Projeto 1: Multiplicador por Somas Consecutivas

8 bits

 


Projeto 1: Multiplicador por Somas Consecutivas

Resultados de Validação:


256 lines (256 sloc) 2.25 KB	
1	00000000
2	00000000
3	00000000
4	00000000
5	00000000
6	00000000
7	00000000
8	00000000
9	00000000
10	00000000
11	00000000
12	00000000
13	00000000
14	00000000
15	00000000
16	00000000
17	00000000
18	00000001
19	00000010
20	00000011
21	00001000
22	00001001
23	00001010
24	00001011
25	00001000
26	00001001
27	00001010
28	00001011
29	00001100
30	00001101
31	00001110
32	00001111
33	00000000

257 lines (257 sloc) 2.29 KB	
1	00000000
2	00000000
3	00000000
4	00000000
5	00000000
6	00000000
7	00000000
8	00000000
9	00000000
10	00000000
11	00000000
12	00000000
13	00000000
14	00000000
15	00000000
16	00000000
17	00000000
18	00000001
19	00000010
20	00000011
21	00001000
22	00001001
23	00001010
24	00001011
25	00001000
26	00001001
27	00001010
28	00001011
29	00001100
30	00001101
31	00001110
32	00001111
33	00000000


Projeto 2: Multiplicador Shifter

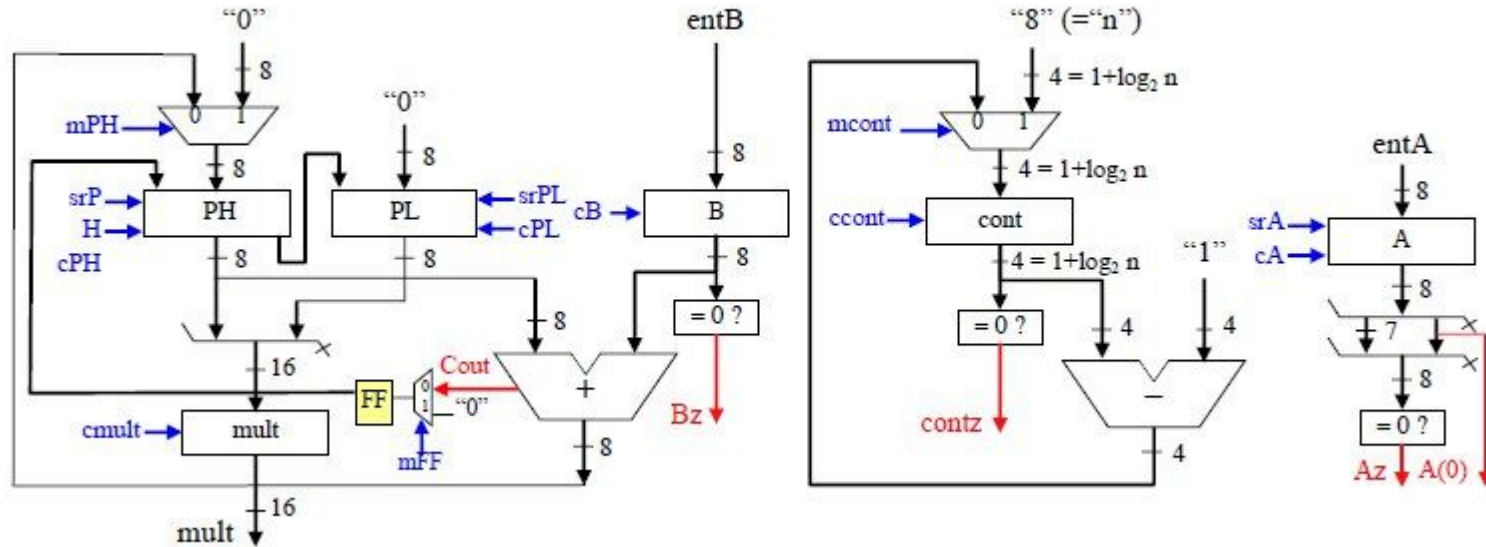


Projeto 2: Multiplicador Shifter (4 bits)

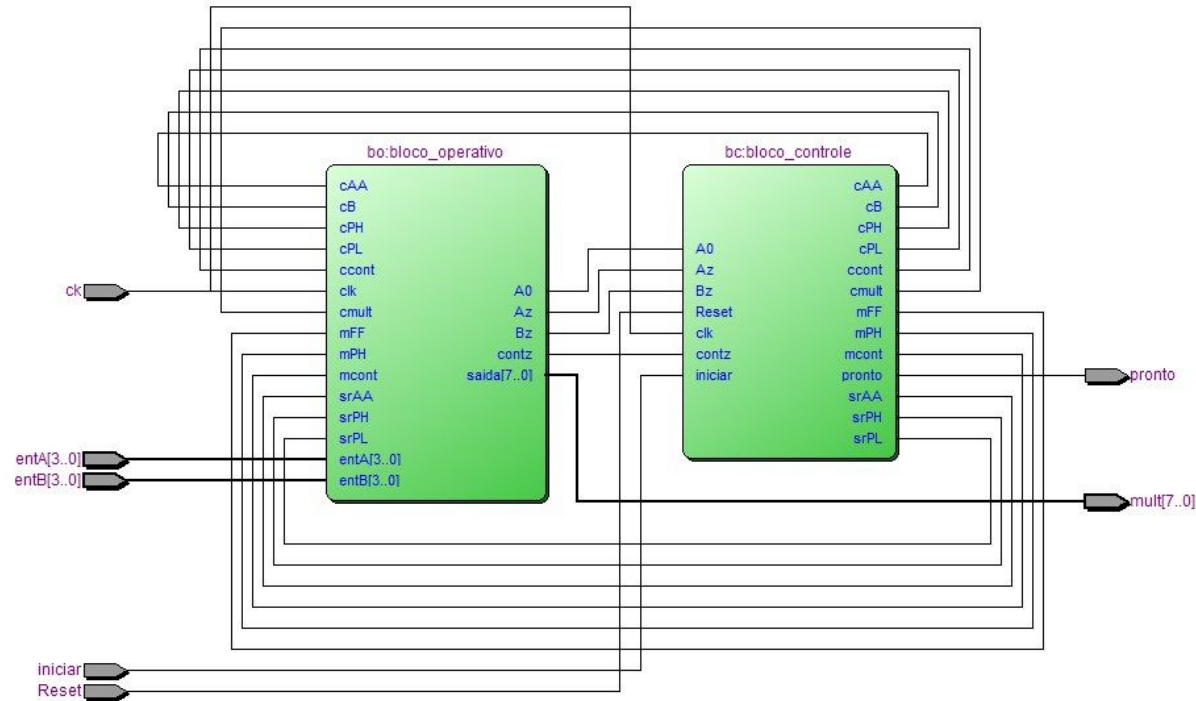

Projeto 2: Multiplicador Shifter (4 bits)

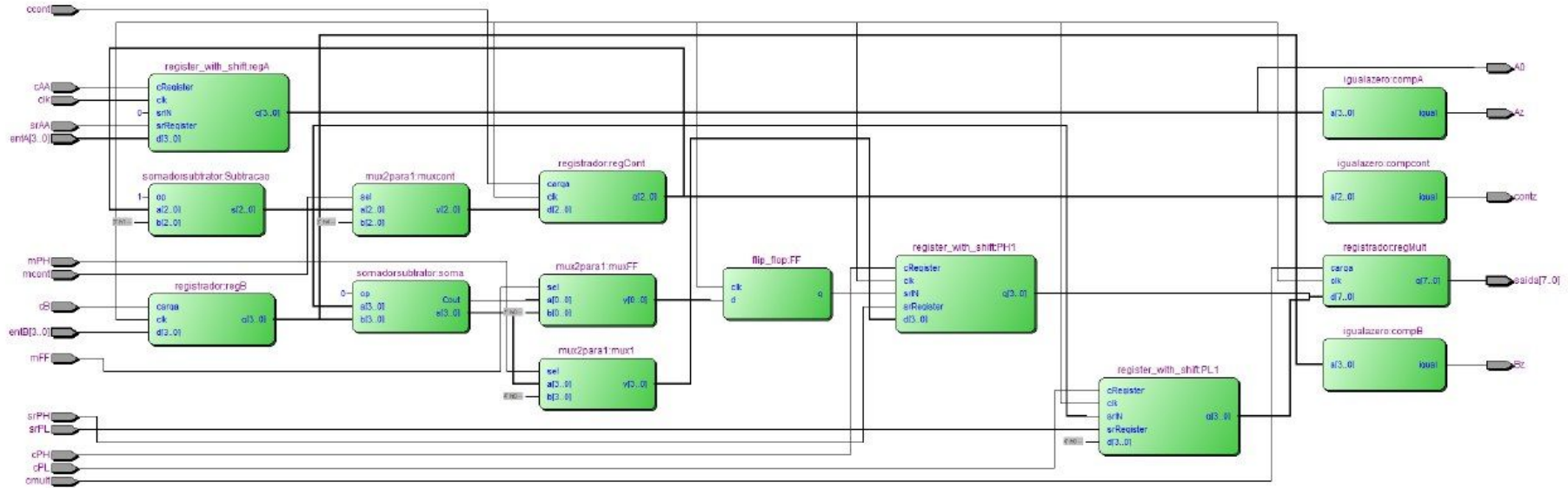


Projeto 2: Multiplicador Shifter (4 bits)

 


Projeto 2: Multiplicador Shifter (8 bits)

Netlists:

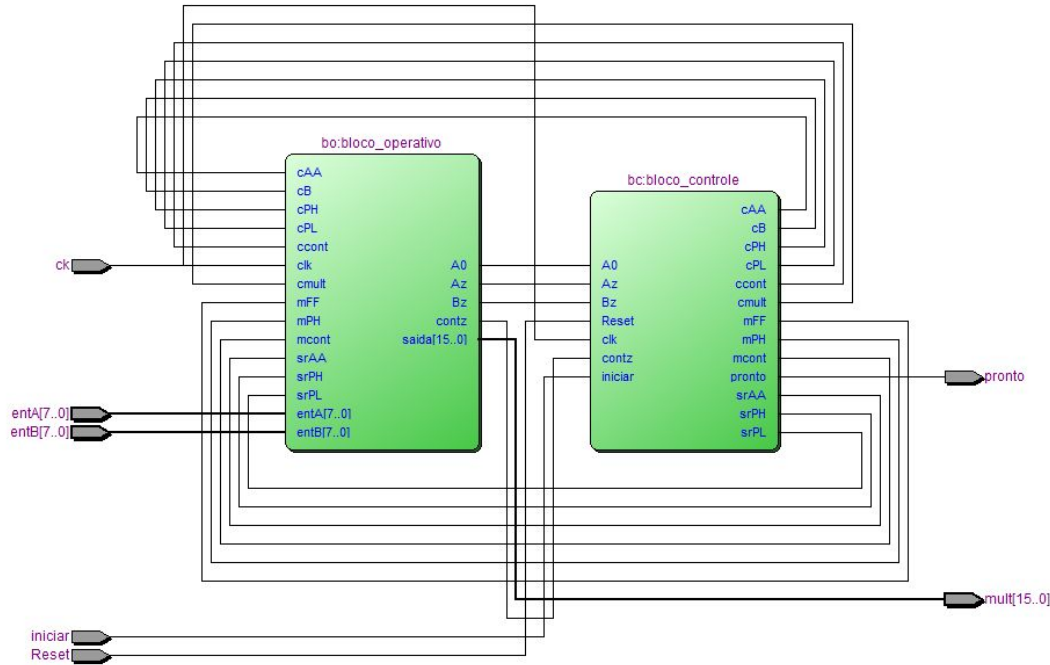


Projeto 2: Multiplicador Shifter (8 bits)


Netlists:

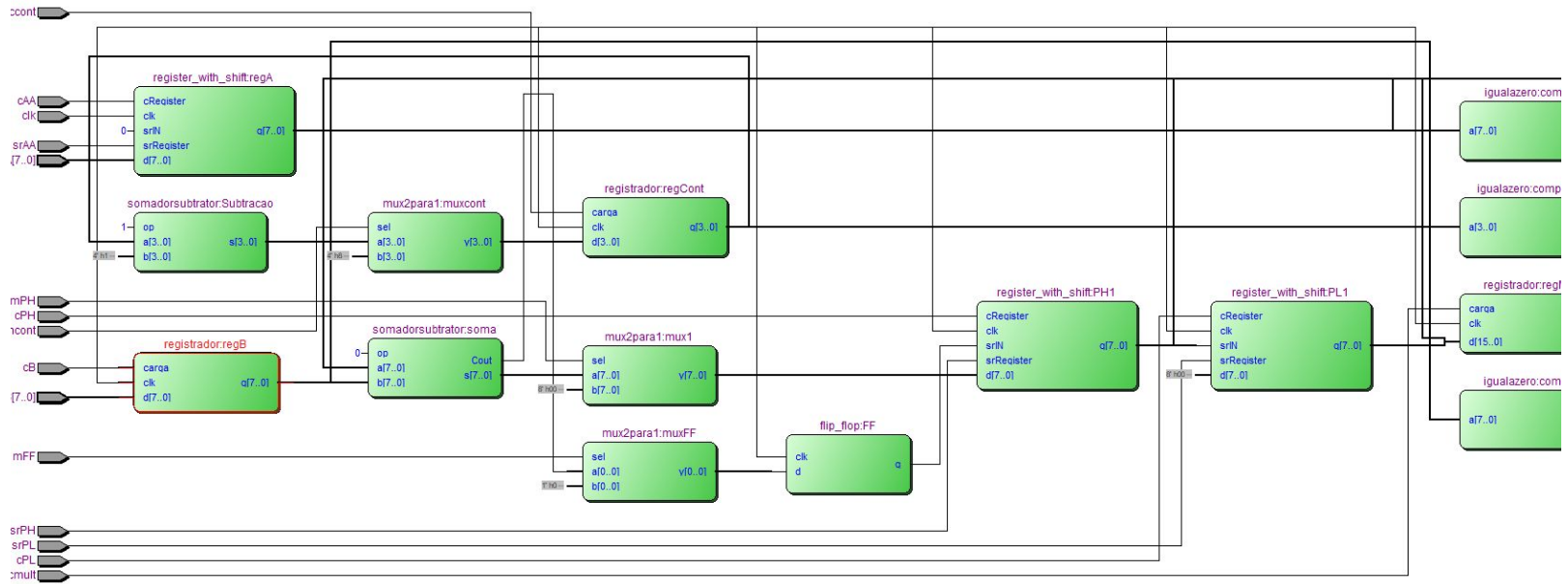


Projeto 2: Multiplicador Shifter (8 bits)

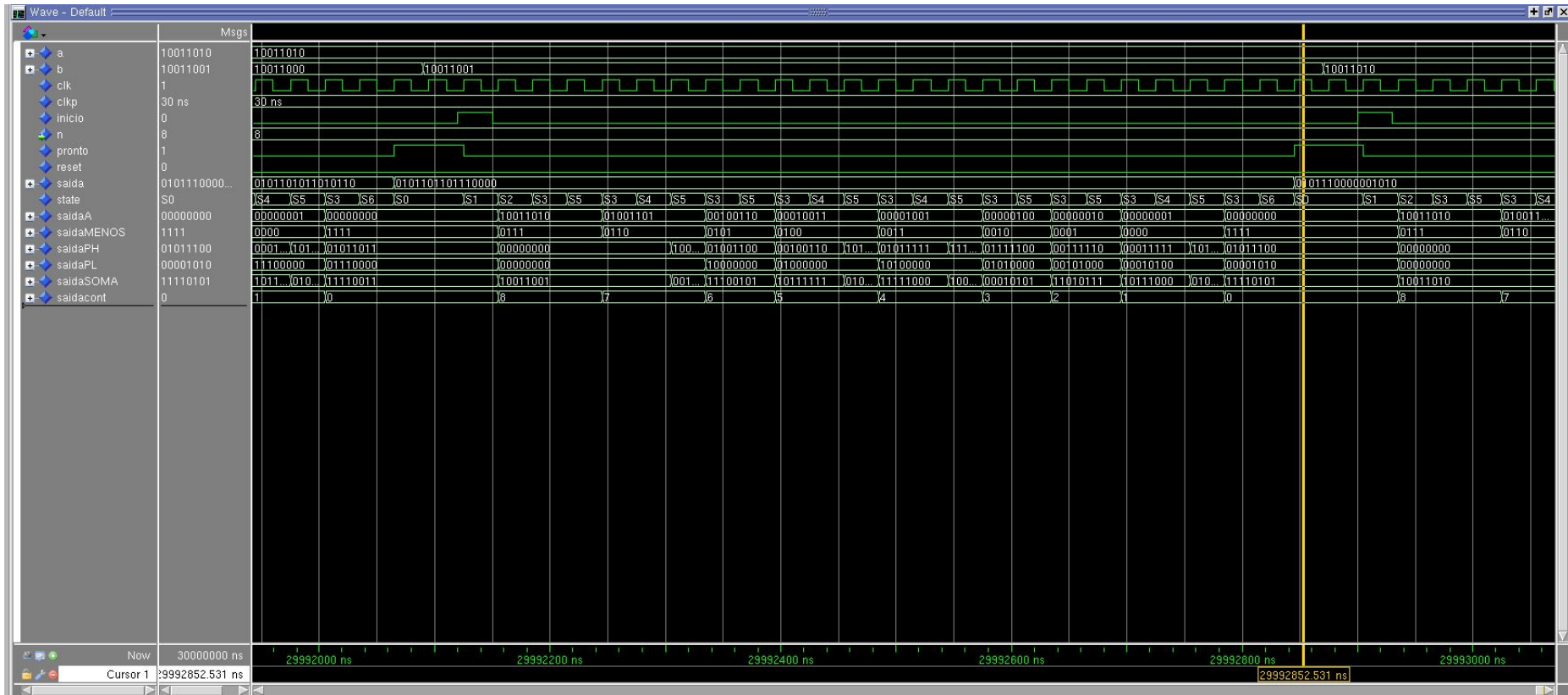


Projeto 3: Multiplicador por Somas Consecutivas Otimizado

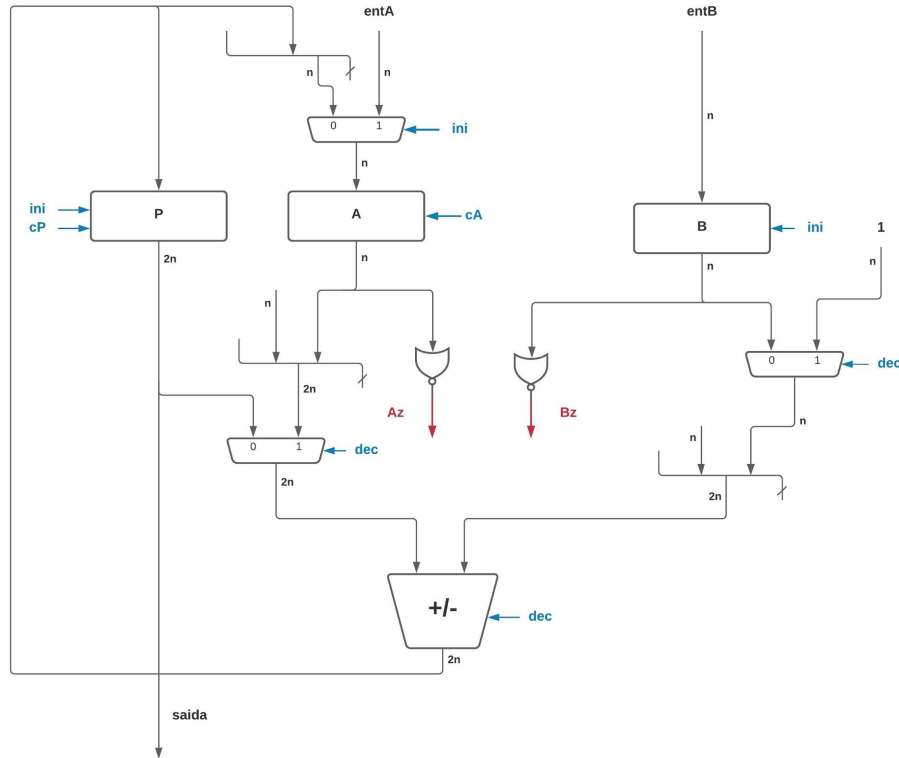


Projeto 3: Multiplicador por Somas Consecutivas Otimizado(4 bits)

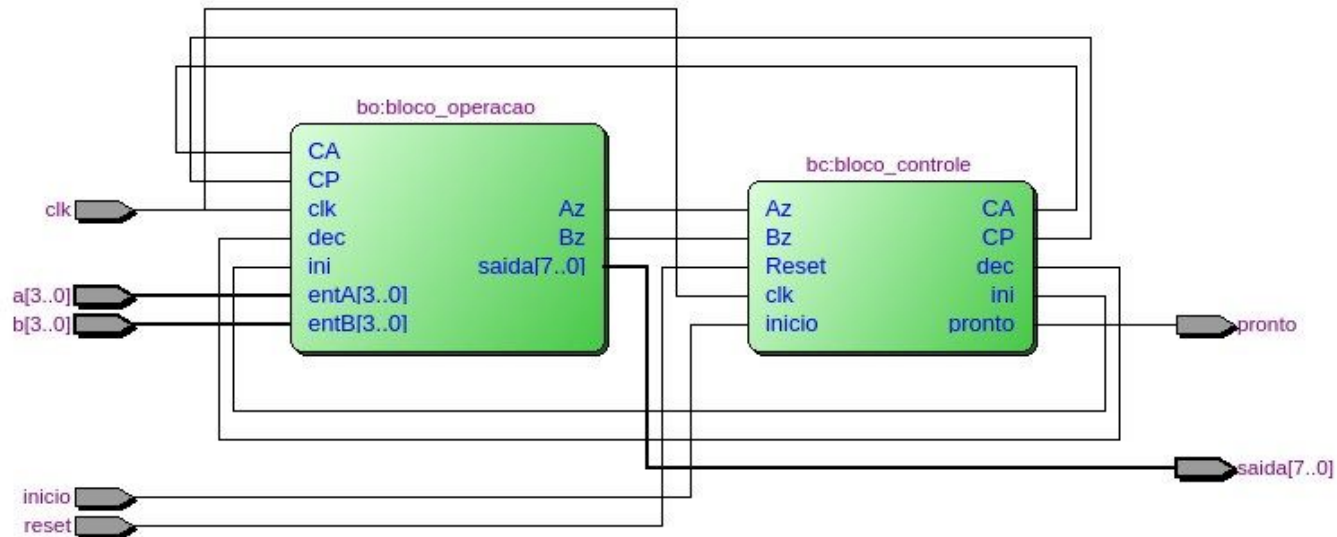

Projeto 3: Multiplicador por Somas Consecutivas Otimizado(4 bits)

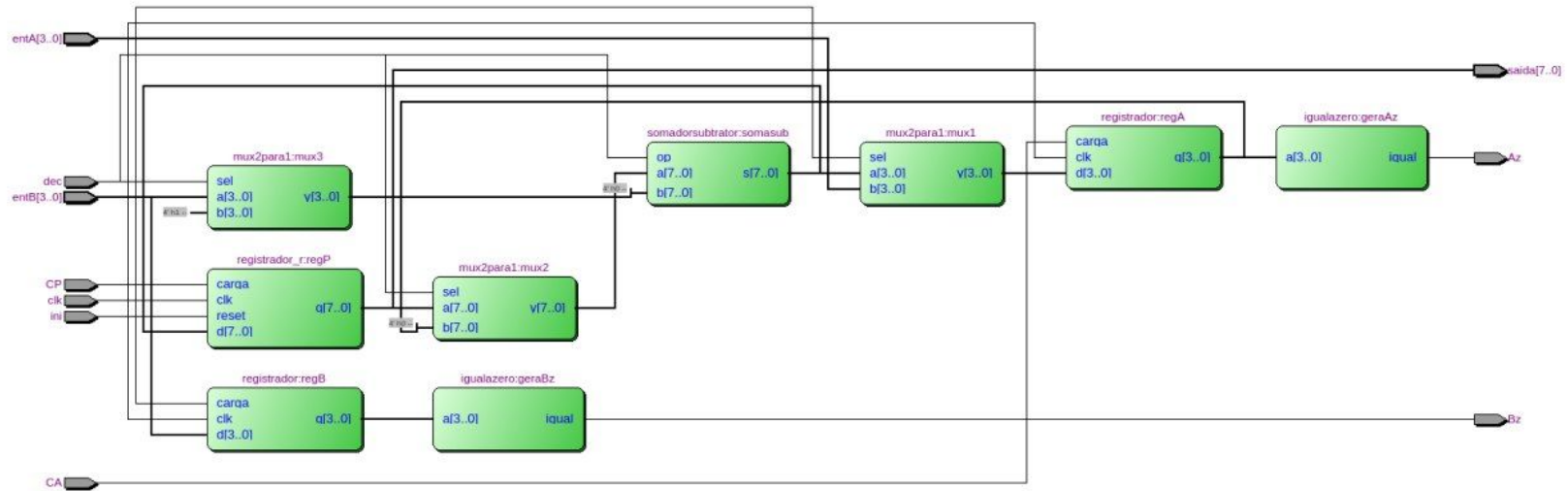


Projeto 3: Multiplicador por Somas Consecutivas Otimizado(4 bits)

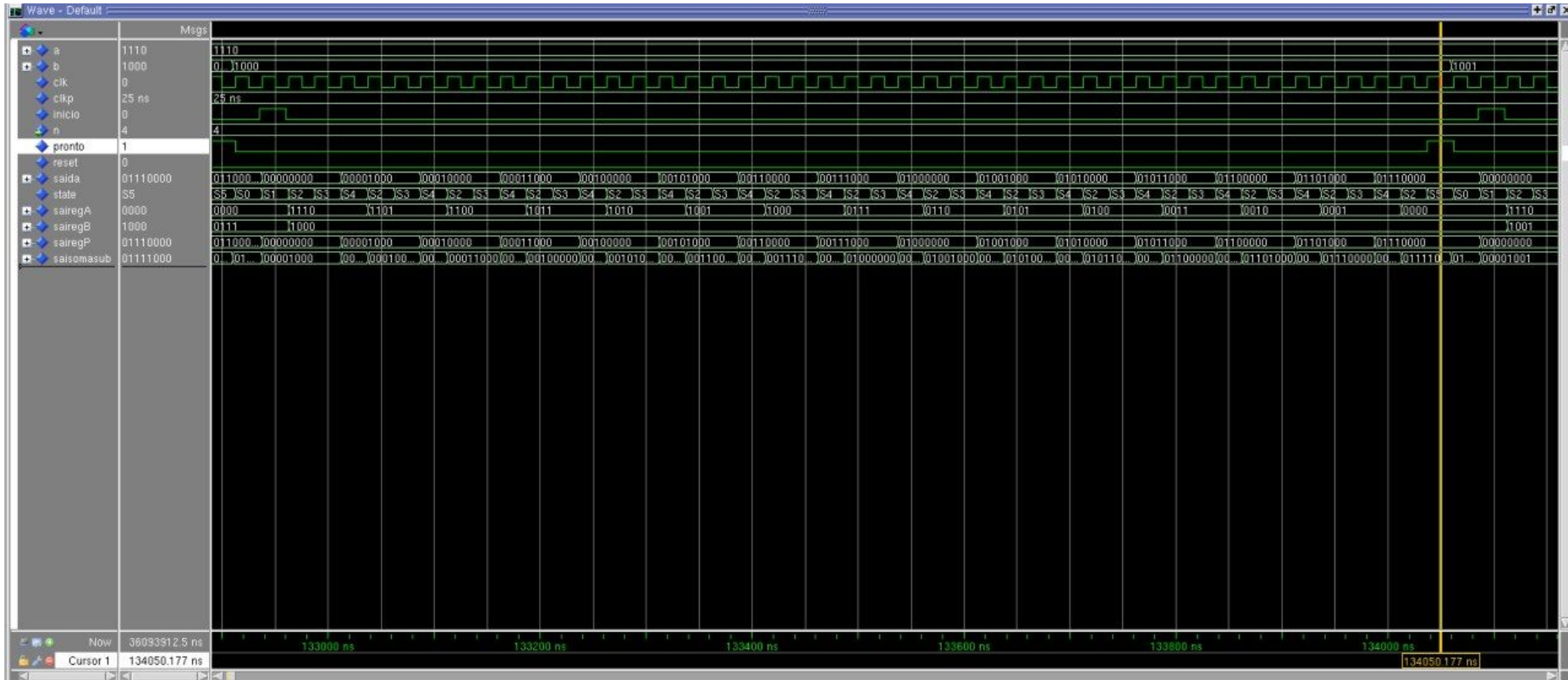


Projeto 3: Multiplicador por Somas Consecutivas Otimizado(8 bits)

Netlists:

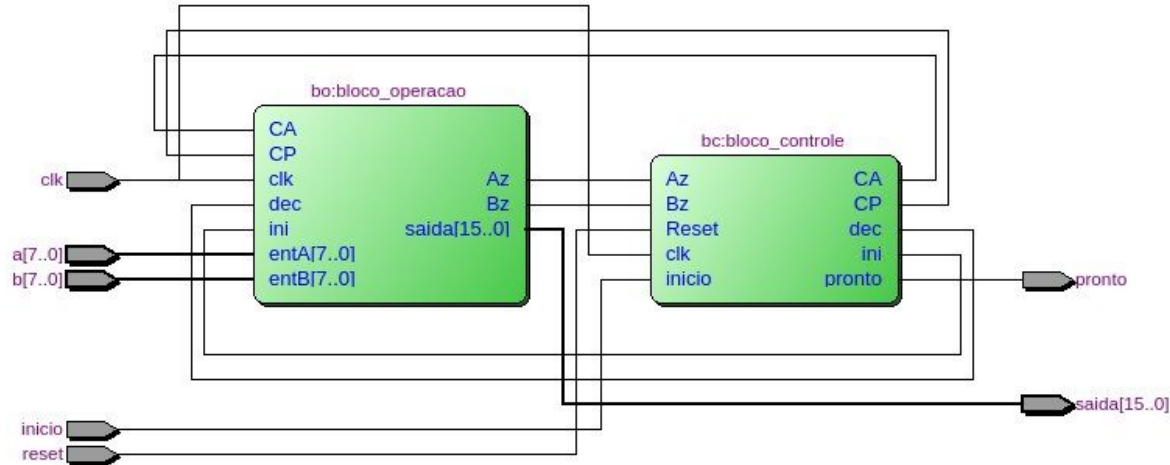


Projeto 3: Multiplicador por Somas Consecutivas Otimizado(8 bits)

Netlists:

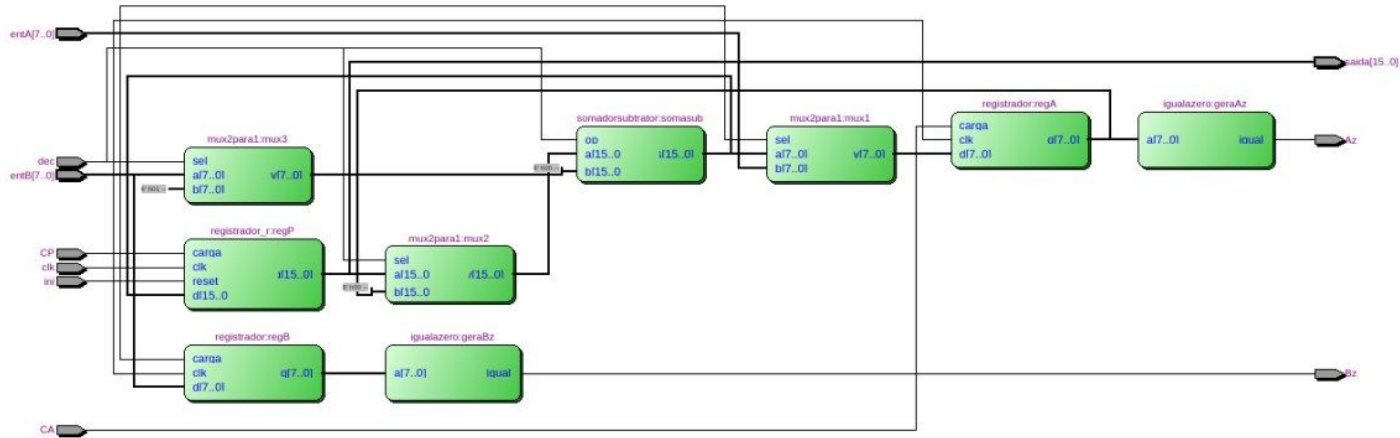

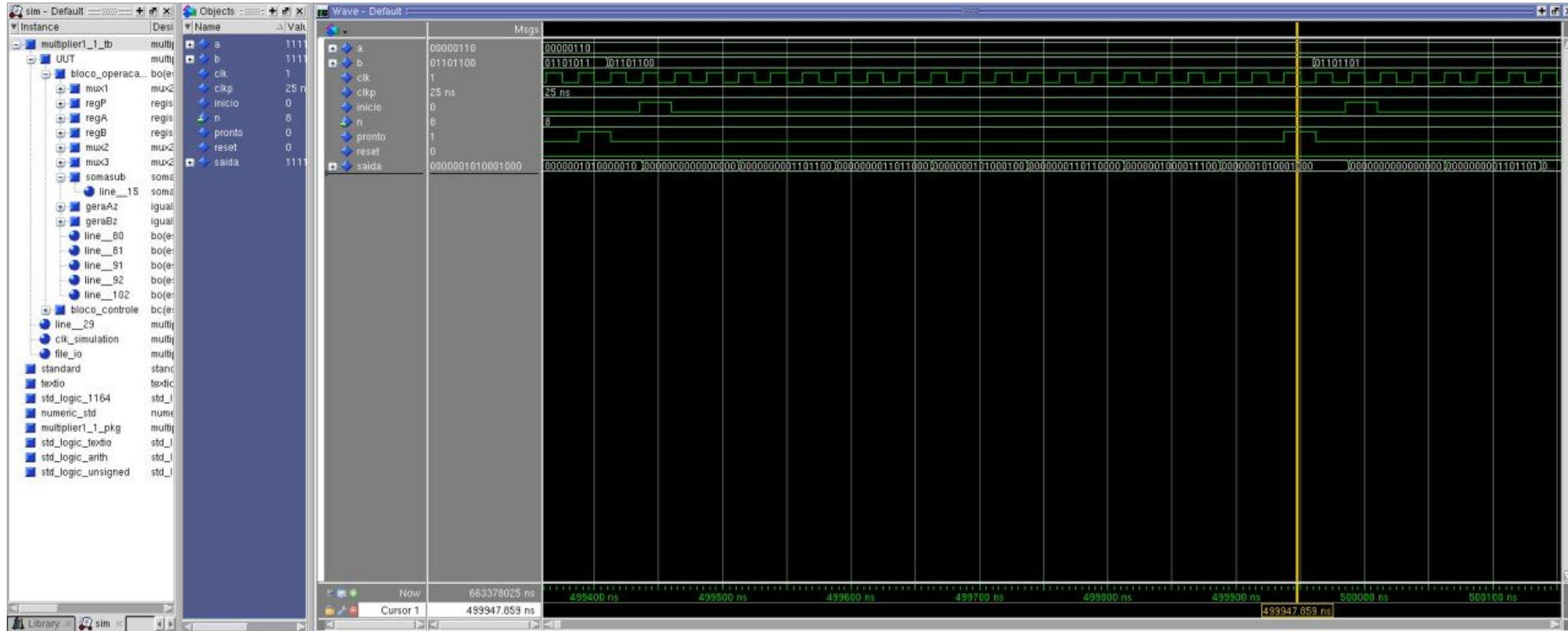Projeto 3: Multiplicador por Somas Consecutivas Otimizado(8 bits)



Comparativos(8 bits):

Numero 1:

Flow Summary	
Flow Status	Successful - Thu Nov 12 02:04:03 2020
Quartus II 64-Bit Version	13.0.0 Build 156 04/24/2013 SJ Web Edition
Revision Name	multiplier1
Top-level Entity Name	multiplier
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	86 / 33,216 (< 1 %)
Total combinational functions	81 / 33,216 (< 1 %)
Dedicated logic registers	54 / 33,216 (< 1 %)
Total registers	54
Total pins	52 / 475 (11 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)

Numero 2:

Flow Summary	
Flow Status	Successful - Thu Nov 12 00:58:24 2020
Quartus II 64-Bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition
Revision Name	multiplier2
Top-level Entity Name	multiplier2
Family	Cyclone II
Total logic elements	72 / 4,608 (2 %)
Total combinational functions	54 / 4,608 (1 %)
Dedicated logic registers	60 / 4,608 (1 %)
Total registers	60
Total pins	36 / 89 (40 %)
Total virtual pins	0
Total memory bits	0 / 119,808 (0 %)
Embedded Multiplier 9-bit elements	0 / 26 (0 %)
Total PLLs	0 / 2 (0 %)
Device	EP2C5T144C6
Timing Models	Final

Numero 3:

Flow Summary	
Flow Status	Successful - Thu Nov 12 01:05:26 2020
Quartus II 64-Bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition
Revision Name	multiplier1_1
Top-level Entity Name	multiplier1_1
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	66 / 33,216 (< 1 %)
Total combinational functions	59 / 33,216 (< 1 %)
Dedicated logic registers	38 / 33,216 (< 1 %)
Total registers	38
Total pins	36 / 475 (8 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)